

**Note:** To get the full mark, you need to show all the steps in details (Final answers are not acceptable).

**Question 1:** Show **algebraically** that the following equation is valid

$$A'BC'D' + (A' + BC) \cdot (A + C'D') + BC'D + A'BC' = ABCD + A'C'D' + ABD + ABCD' + BC'D$$

State which theorem you have used for each step in your work.  
(Hint: simplify the LHS first, and then simplify the RHS of the equation.)

**Question 2:** Simplify the following expression to a minimum number of literals(variables) and terms using boolean algebra theorems

$$ab'cd'e + acd + acf'gh' + abcd'e + acde' + e'h'$$

State which theorem(s) you have used for each step in your work.

**Question 3:** Design an error detector for 6 – 3 – 1 – 1 binary-coded-decimal digits. The output ( $F$ ) is to be 1 **iff** the four inputs ( $A, B, C, D$ ) represent an invalid code combination.

- Build the truth table for the error detector.
- Find the min-terms expansion of the function  $F$ .
- Simplify the function  $F$  using Boolean algebra theorems to **two terms**.
- Construct the logic circuit of the simplified function  $F$ .

**Question 4:** Given the function  $f(a, b, c, d) = a'(b' + d) + acd'$ , then:

- Find the min-term expansion of the function  $f$ .
- Find the max-term expansion of the function  $f$ .

**Question 5:** Simplify the following expression to two terms using boolean algebra theorems

$$AB' + A'C'D' + A'B'D + A'B'CD'$$

State which theorem(s) you have used for each step in your work.

**Question 6:** Simplify the following expression to a minimum number of terms, and at the same time, the simplified expression shall be expressed in POS format. Use boolean algebra theorems.

$$CD + AB' + AC + A'C' + A'B + C'D'$$

State which theorem(s) you have used for each step in your work.

**Question 7:** Simplify each of the following expressions to a minimum number of terms, and at the same time, each term shall consists of a minimum number of variables. Use boolean algebra theorems.

(a)  $XY + X'YZ' + YZ$

(b)  $XY' + Z + (X' + Y)Z'$

(b)  $(XY' + Z)(X + Y')Z$

State which theorem(s) you have used for each step in your work.

-----

The problems below are from the Textbook (5<sup>th</sup> edition):

**Question 8.** Problem 2.2 (e) and 2.2 ( f)

**Question 9.** Problem 2.8

**Question 10.** Problem 2.9 (c)

**Question 11.** Problem 2.13 (c) using NOR only and 2.13 (e) using only NAND

**Question 12.** Problem 2.17 (d)