

CE2120-Digital Systems Lab

Lab 9

I. Objectives

The objective of this lab is to become familiar with latches and clocked flip-flops, and building one F.F. using other type of F.F.'s.

II. Preparations

1. A characteristic equation gives the next state of a latch in terms of the inputs and the current state. Derive the characteristic equation for the J-K and the D latches, then find the following for both J-K and D latches:
 - a. Build the next state table.
 - b. Using the next state table in part a, construct a k-map for each latch and find its characteristic equation.
 - c. Draw the logic circuit of each latch.
2. Convert a clocked D flip-flop (74LS74) to a clocked T flip-flop.
 - a. Derive an expression for D in terms of T and Q.
 - b. Draw the logic diagram of the circuit.
3. Convert a clocked D flip-flop (74LS74) to a clocked JK flip-flop.
 - a. Derive an expression for D in terms of J, k and Q.
 - b. Draw the logic diagram of the circuit.
4. Design a 3-bit synchronous counter $0 \rightarrow 1 \rightarrow 2 \rightarrow 4 \rightarrow 7$ and back to zero. Obtain the state transition table and the K-Map's for each flip-flop input. Use JK flip-flop (74LS76, if not available use 74LS73). Draw the logic diagram of the counter

III. Lab work

In this experiment:

- a. Setup the circuits in part 1 on your breadboard and check its operation.
- b. Setup the circuits in part 2 on your breadboard and check its operation.
- c. Setup the circuit in part 3, on your breadboard and check its operation.
- d. Setup the circuit in part 4, on your breadboard and check its operation.