### **CE2120**

## **Digital Systems**

### Lab 7

## **Hashem Qaryouti**

### 20201502049


## Question 1


#### a.

S	l1	10	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$F(S,I1,I0) = \sum_{m} (1,3,6,7)$$

$$F = S'IO + SI1$$

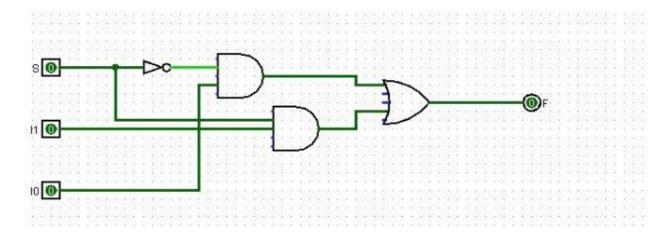

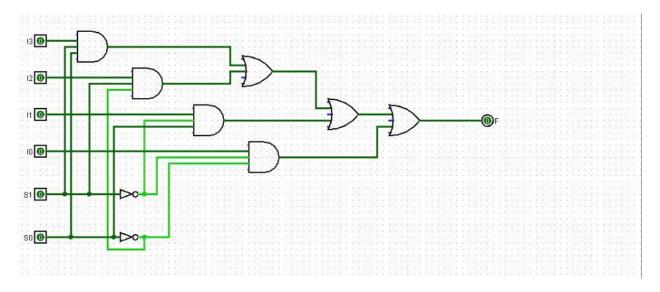



$$F(x,y,z) = xz'+xy+x'y'z$$

=m6=+m4+m7+m4+m1

$$F(x,y,z) = \sum_{m} (1,4,6,7)$$


X	Υ	Z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

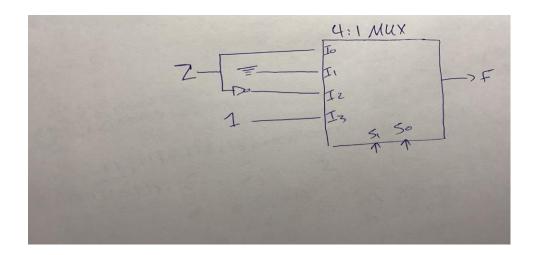

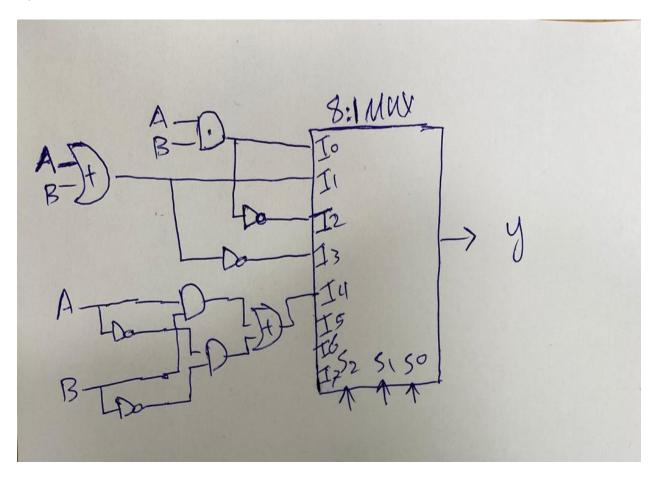

E	D	Α	В
0	0	0	0
0	1	0	0
1	0	0	0
1	1	0	1

$$B(E,D) = m3 = (E+D)'' = (E'+D')'$$

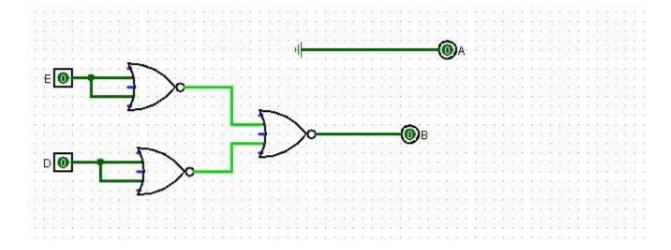

D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>	Y <sub>0</sub>	Y <sub>1</sub>	Y <sub>2</sub>	Y <sub>3</sub>	Y <sub>4</sub>	<b>Y</b> <sub>5</sub>	<b>Y</b> <sub>6</sub>	<b>Y</b> <sub>7</sub>
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

