

Digital Systems Lab

CE2120

Lab 9

Hashem Qaryouti

20201502049


Question 1

a.

J	K	Q(t)	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

D	Q(t)	Q(t+1)
0	0	0
0	1	0
1	0	1
1	1	1

b.


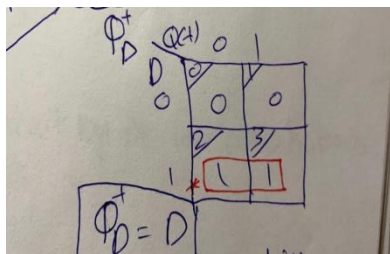


ϕ^+
 JK JK
 $Q(t)$

$Q(t)$	00	01	11	10
0	0	0	1	1
1	1	0	0	1

ϕ^+
 $P_{JK}^+ = \bar{J} \cdot \bar{Q}(t) + \bar{K} \cdot Q(t)$

c.

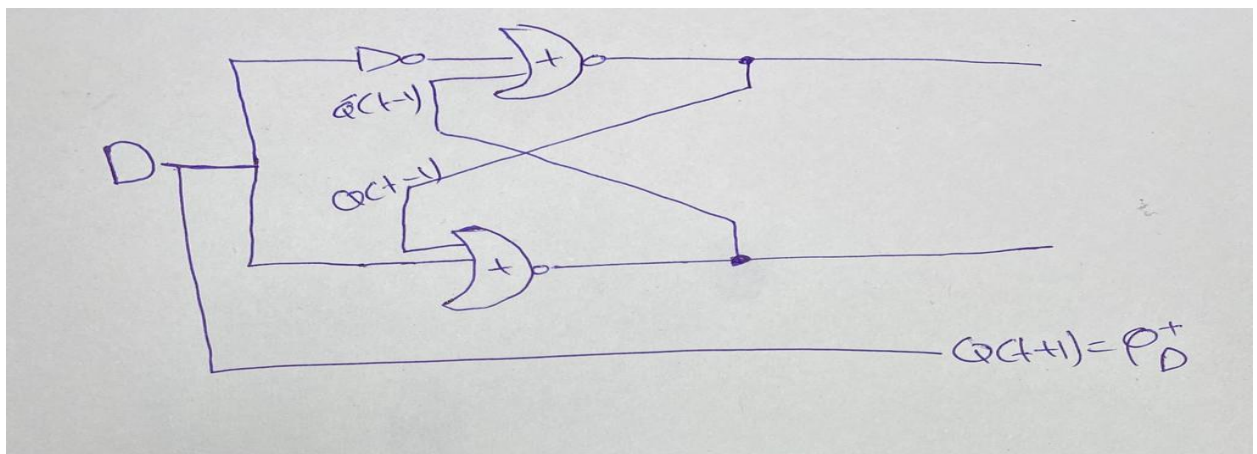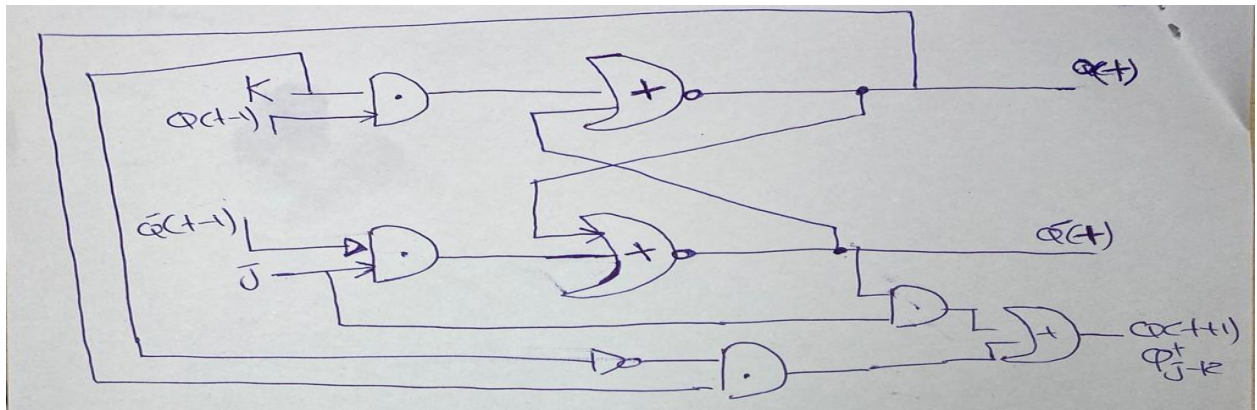

Question 2

a. step1: Build the next state table of the T f.f

T	Q(t)	Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0

Step2: Build the excitation table of the D f.f


Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1

Step3: Add a column for each input of the building block f.f to the next state table of the f.f we want to build

T	Q(t)	Q(t+1)	D
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

$$D(T, Q(t)) = T \text{ XOR } Q(t)$$

b.

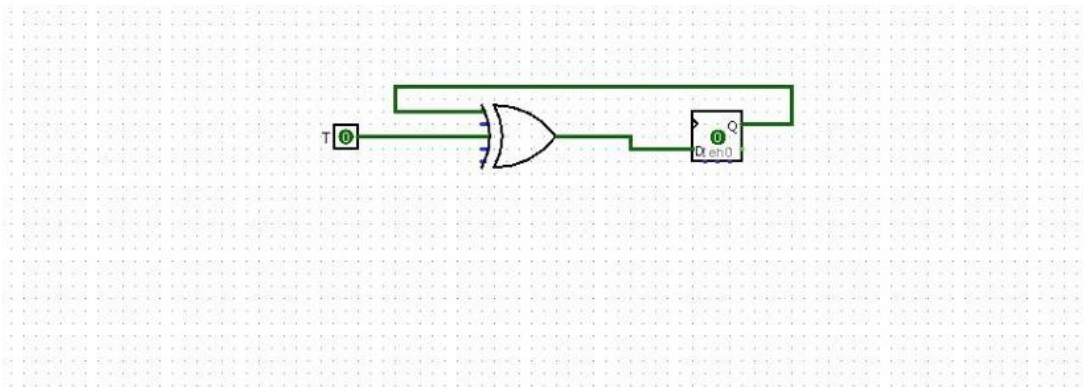

Question 3

a. step1: Build the next state table of the T f.f

J	K	Q(t)	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Step2: Build the excitation table of the D f.f


Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1

Step3: Add a column for each input of the building block f.f to the next state table of the f.f we want to build

J	K	Q(t)	Q(t+1)	D
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	0	0
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	0	0

$$D(J,K,Q(t)) = K'.Q(t) + J.Q'(t)$$

b.

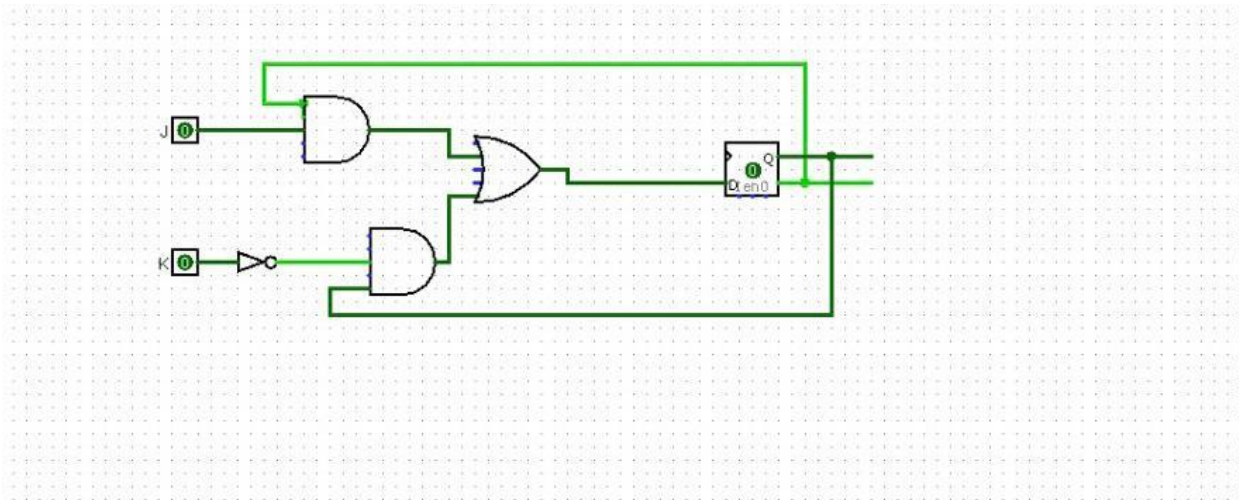

Question 4

Step1: we need 3 J-K F.Fs

Step2 : Sate table

QA	QB	QC	QA ⁺	QB ⁺	QC ⁺
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	X	X	X
1	0	0	1	1	1
1	0	1	X	X	X
1	1	0	X	X	X
1	1	1	0	0	0

Step 3: Transition table

QA	QA	QA	QA ⁺	QB ⁺	QC ⁺	JA	KA	JB	KB	JC	KC
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
0	1	1	X	X	X	X	X	X	X	X	X
1	0	0	1	1	1	X	0	1	X	1	X
1	0	1	X	X	X	X	X	X	X	X	X
1	1	0	X	X	X	X	X	X	X	X	X
1	1	1	0	0	0	X	1	X	1	X	1

Step 4 : f.fs inputs equation

JA KBAQC

QA	00	01	11	10
0	0	0	X	1
1	X	X	X	X

$JA = QB$

KA QBQC

QA	00	01	11	10
0	X	X	X	X
1	0	X	1	X

$KA = QB$

JB QBQC

QA	00	01	11	10
0	0	1	X	X
1	1	X	X	X

$JB = QA + QC$

KB QBQC

QA	00	01	11	10
0	X	X	X	1
1	X	X	1	X

$KB = 1$

JC QBQC



QA	00	01	11	10
0	1	X	X	0
1	1	X	X	X

$JC = QB$

KC QBQC

QA	00	01	11	10
0	X	1	X	X
1	X	X	1	X

$KC = 1$

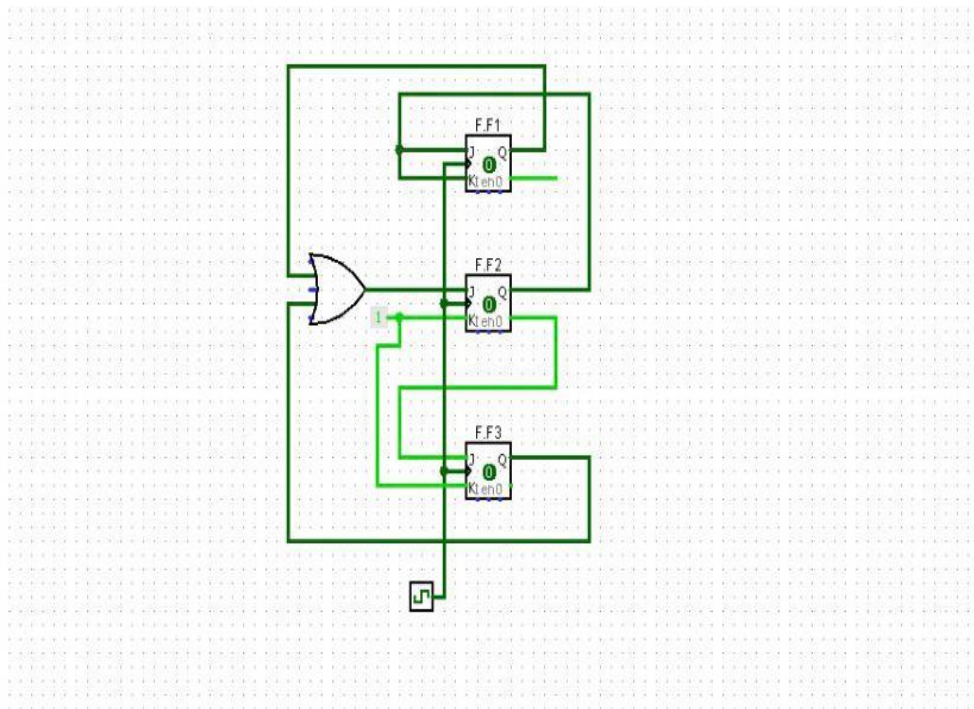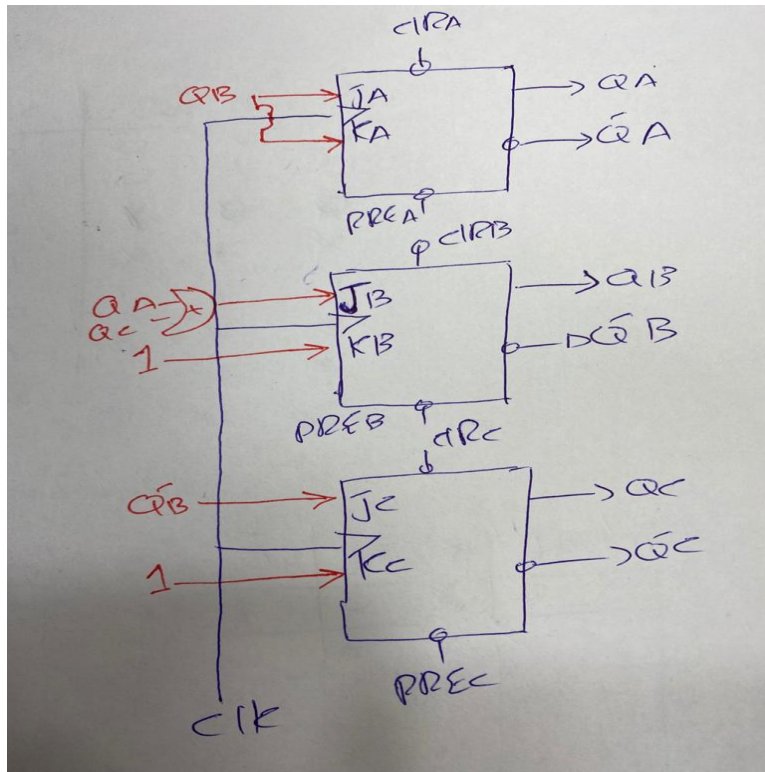

Unused States

QA QB QC = 0 1 1

To be in this state

CLR_A=PRE_B=PRE_C= 0

CLR_B=PRE_A= CLR_C = 1

To proceed, deactivate all clears and presets inputs

Rising edge : 0 1 1 → 1 0 0

JA= KB = 1 → toggle operation

JB = KB = 1 → toggle operation

JC = KC = 0 → reset operation

QA QB QC = 1 0 1

Rising edge : 1 0 1 → 1 1 0

JA= KB = 0 → Buffer operation

JB = KB = 1 → toggle operation

JC = KC = 1 → toggle operation

QA QB QC = 1 1 0

Rising edge : 1 1 0 → 0 0 0

JA= KB = 1 → toggle operation

JB = KB = 1 → toggle operation

JC =0, KC = 1 →Reset operation
