

CE2120 - Digital Systems Lab


Lab 10

I. Objectives

The objective of this lab is to construct and analyze synchronous sequential circuits using state table and state transition diagram.

II. Preparations

- Given the sequential circuit below:

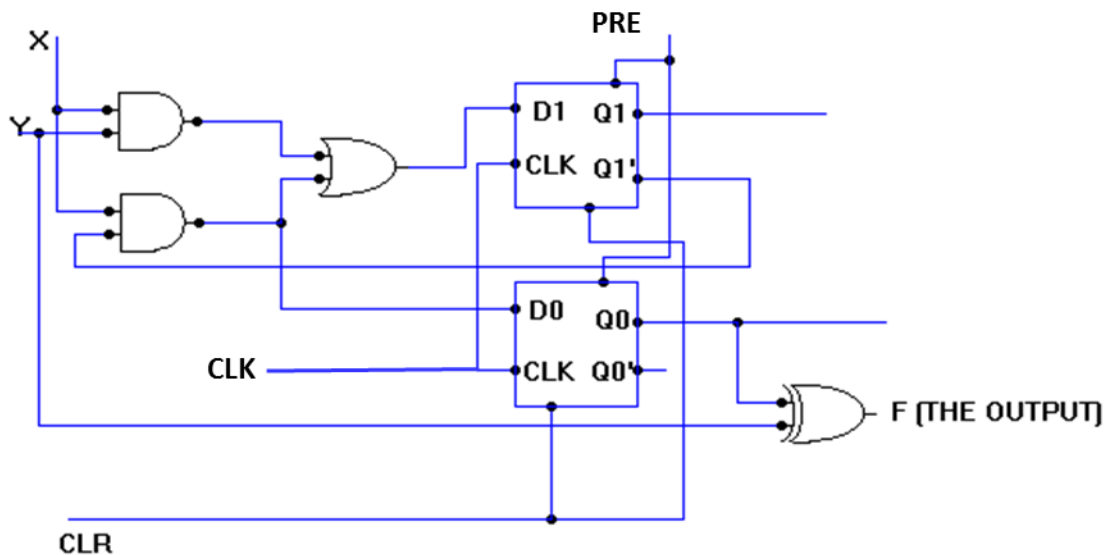

- Determine whether the circuit above is a Mealy or a Moore machine.
 - Construct the state transition table of this state machine.
 - Construct the state graph of this state machine.
- Draw the logic diagram of a 3-bit parallel in parallel out register with mode selection inputs S_0 and S_1 . The register operates according to the following function table.

S_0	S_1	Register operation
0	0	No change
0	1	Complement outputs
1	0	Clear register to 0
1	1	Load parallel data

Use D-flip flops, 4:1 Multiplexers, and any combinational circuit that is required to implement the operations specified above. Identify your inputs, outputs, and control signals labels clearly.

III. Lab work

In this experiment:

- a. Setup the circuits in part 1 on your breadboard and check its operation.
- b. Setup the circuits in part 2 on your breadboard and check its operation.