

# CE2120-Digital Systems Lab

## Lab 7

### **I. Objectives**

The objective of this lab is to become familiar with Decoders and Multiplexers, and to use them to construct Boolean functions.

### **II. Preparations**

1. A  $2^n : 1$  MUX has  $2^n$  data input,  $n$  control input, and 1 data output. It selects one of the data inputs and connects to its output depending on the value of the control input.
  - a. Design a 2:1 MUX using **logic gates**.
  - b. Build a 4:1 MUX which has 4 data inputs, 2 control inputs, and 1 output **using an appropriate number of the 2:1 MUX(s) you have designed in part (a)**.

For each part, show the truth table and provide a Boolean expression for the MUX output. Also, draw the logic circuit for each part.

2. An  $n : 1$  multiplexer can be used to implement a logic function with  $(n+1)$  variables **without additional gates**. Implement the function  $F$  using a 4:1 MUX (74LS153)

$$F(X, Y, Z) = XZ' + XY + X'Y'Z$$

Show the design of your logic circuit and obtain the truth table for this function.

3. Design a logic unit that performs logical operation on two 1-bit inputs depending on the value of the 3 selection inputs. The required functions are AND, OR, NAND, NOR, and XNOR. Draw the logic circuit that performs the required functionality **using 8:1 MUX (74LS152) and additional gates**.
4. Design a 1:2 decoder with enable input **using NOR gates**. Provide the truth table and the logic circuit of your design.
5. Design a 3:8 decoder using 2:4 decoders (74LS139). Provide the truth table and the logic circuit of your design

### ***III. Lab work***

In this experiment:

- a. Setup the circuits in part 1.a and 1.b on your breadboard and check its operation.
- b. Setup the circuit in 2 on your breadboard and use LEDs to check the logic level of the outputs. Also, check the operation of the circuit using the obtained truth table.
- c. Setup the circuit in 3 on your breadboard and use LEDs to check the logic level of the outputs. Also, check the operation of the circuit using the obtained truth table.
- d. Setup the circuit in 4 on your breadboard and use LEDs to check the logic level of the outputs. Also, check the operation of the circuit using the obtained truth table.
- e. Setup the circuit in 5 on your breadboard and use LEDs to check the logic level of the outputs. Also, check the operation of the circuit using the obtained truth table.